



Introduction

The PLL frequency synthesizer has become one of the basic building blocks in modern communications systems. Many monolithic PLL integrated circuits are available, which incorporate the needed frequency dividers and the phase detector. An extremely common phase detector is the charge pump.

It is common practice to use a charge pump phase detector with a passive loop filter such as that shown in Figure 1

 


Figure 1 - Passive Loop Filter

In this configuration the voltage swing available to the VCO is limited to the voltage supplied to the charge pump phase detector. Typical integrated circuit operating voltages have resulted in a 0 to 5V range being commonly available. As chip operating voltages have been decreasing, there are options to reduce this voltage range. This paper describes the detrimental effects on locking performance if the charge pump voltage supply is decreased too far.

Design Example

We will firstly illustrate the problem.

Consider a PLL designed for:
Output frequency range: 100MHz to 130MHz
Channel Spacing: 25kHz
Charge pump current: 1mA
VCO $K_v = 10\text{MHz/V}$

To centre the VCO range, assume that the VCO tunes from 90MHz at 0V to 140MHz at 5V.

Loop bandwidth = 2.5kHz, Phase margin = 45 degrees
 $C1 = 3.68\text{nF}$, $R1 = 8.65\text{k}$, $C2 = 17.8\text{nF}$

The transient response for a frequency step from the bottom of the band to the top of the band is shown in

Figure 2 where it is assumed that the charge pump has unlimited voltage swing. The lock time to within 1kHz is 1.21ms.

 


Figure 2 - 100MHz to 130MHz Transient - no limiting

The simulation in Figure 2 (and all others in this paper) were performed using Applied Radio Labs **SimPLL** software package [1].

If we now introduce saturation in the charge pump output, where we assume that the charge pump cannot deliver charge above 5V or below 0V, the transient response becomes as shown in Figure 3:

 


Figure 3 - Limiting at 0V and 5V

The lock time to 1kHz has increased to 1.38ms. Reducing the upper limiting voltage to 4.5V further increases the lock time to 1.69ms with transient response shown in Figure 4

 


Figure 4 - Limiting at 0.5V and 4.5V

 


Figure 5 - Expanded transient, no saturation

To summarize:

Clipping Level (Volts)	Time to Lock to 1kHz (ms)
None	1.21
5	1.38
4.5	1.69
4.25	2.21

Note that in each case the target steady state voltage on the VCO control line is 4V.

So it can be seen that failing to provide adequate headroom in the charge pump output can lead to significant increases in PLL lock times. It also indicates that normal production variations in VCO tuning law can lead to significant variations in PLL lock time.

Discussion of Effect

The reason for this effect may be readily understood from the loop filter schematic Figure 1 and the unclipped transient in Figure 2. Expanding the early part of the transient we see

In the loop filter in Figure 1,

$$C_1 \approx 0.1C_2$$

At the beginning of the transient, the charge pump supplies current to the loop filter to increase the VCO voltage. During the short phase detector pulses this current flows primarily into C_1 , (the voltage spikes) and in-between the spikes much of the charge from C_1 flows through R_1 to C_2 (the decaying voltage between the spikes). To get a reasonable current flow into C_2 (which is the biggest) necessarily requires the voltage across C_1 to rise to levels significantly above the voltage across C_2 . Limiting these spikes significantly reduces the flow of current into C_2 .

Conclusion

The voltage headroom provided at by the charge pump phase detector can have significant effect on PLL lock time. The lack of sufficient headroom can result in a major degradation of locking performance.

The effect on lock times can be readily determined using a simulation package such as SimPLL.

REFERENCES:

1. SimPLL software package, available at: www.radiolab.com.au (note all simulations in this article can be performed using the free demo version of SimPLL)

For further information visit www.radiolab.com.au,